



If the wall transformer is 5 VDC, then use a 470 Ohm resistor.
If the wall transformer is 12 VDC, then use a 1K resistor

You will need:

- One 5 VDC or 12 VDC wall transformer
(this transformer will power several LED signals)
- One Red LED
- One Green LED
- One 470 Ohm, 1/4 Watt or one 1K Ohm, 1/4 Watt resistor