

## Using a Dual Relay to Control Staging Track Power

Version 2 – September 23, 2014

Each half of a Dual Relay can independently control power (on/off) to one track feeder wire as shown below. One wire of the track bus is fed into the Common terminal of J3 on the Dual Relay and out the Normally Closed (NC) terminal. Power can then be turned on or off by using a stationary accessory decoder to control the relay.

